

California State University, Fresno
Lyles College of Engineering
Department of Electrical and Computer Engineering

TECHNICAL REPORT

Project Title: Mips Processor

Course Title: ECE 174 Advanced Computer Engineering

Date Submitted: May 18, 2023

Course Instructor: Dr. El Razouk

| Prepared By | Section Written |
|----------------------|---------------------------------|
| Omer Al Sumeri | Abstract, Conclusion |
| Aryan Singh | Literature Review, Procedure |
| Luigi Santiago-Villa | Theoretical Background, Results |

INSTRUCTOR SECTION

Comments:

Final Grade: Omer Al Sumeri :
Aryan Singh :
Luigi Santiago-Villa:

TABLE OF CONTENTS

| | |
|---|-----------|
| 1. Abstract..... | 4 |
| 2. Literature Review..... | 4 |
| 3. Theoretical Background..... | 4 |
| 4.1 Instruction Stage Modules..... | 8 |
| 4.2 Control Module..... | 8 |
| 4.3 Register File..... | 9 |
| 4.4 Forwarding Unit..... | 10 |
| 4.5 Hazard Detection Unit..... | 11 |
| 4.6 ALU Module..... | 12 |
| 4.7 Data Memory..... | 12 |
| 4.8 Single Cycle Implementation..... | 13 |
| 4.9 Pipeline Registers..... | 14 |
| 4.10 Pipelined Implementation (Top Module)..... | 15 |
| 4.11 Equipment Used..... | 15 |
| 5. Results..... | 16 |
| 5.1 Load Word Instruction Simulation..... | 16 |
| 5.2 Store Word Simulation Results..... | 17 |
| 5.3 Add Simulation Results..... | 18 |
| 5.4 Add Immediate Simulation Results..... | 19 |
| 5.5 And Simulation Results..... | 19 |
| 5.6 Nor Simulation Results..... | 20 |
| 5.7 Or Simulation Results..... | 21 |
| 5.8 Set-Less-Then Simulation Results..... | 22 |
| 5.9 Subtraction Simulation Results..... | 23 |
| 5.10 Multiplication Simulation Results..... | 24 |
| 5.11 Division Simulation Results..... | 26 |
| 5.12 Forwarding Unit Simulation Results..... | 27 |
| 5.13 Hazard Unit Simulation Results..... | 28 |
| 5.14 Branch If Equal Simulation Results..... | 29 |
| 5.15 Jump Instruction Simulation Results..... | 29 |
| 5.16 Synthesization Results..... | 30 |
| 6. Conclusion..... | 30 |
| 7. References..... | 31 |
| 8. Appendices..... | 32 |
| Appendix A..... | 32 |
| Appendix B..... | 33 |
| Appendix C..... | 34 |
| Appendix D..... | 36 |
| Appendix E..... | 37 |
| Appendix F..... | 38 |
| Appendix G..... | 39 |
| Appendix H..... | 40 |

| | |
|-----------------|----|
| Appendix I..... | 41 |
| Appendix J..... | 42 |
| Appendix K..... | 43 |
| Appendix L..... | 44 |
| Appendix N..... | 47 |
| Appendix O..... | 49 |
| Appendix P..... | 50 |
| Appendix Q..... | 51 |
| Appendix R..... | 52 |
| Appendix S..... | 53 |
| Appendix T..... | 54 |
| Appendix U..... | 55 |
| Appendix V..... | 56 |
| Appendix W..... | 57 |
| Appendix X..... | 58 |
| Appendix Y..... | 59 |
| Appendix Z..... | 60 |

1. Abstract

The objective of this project is to design and implement a processor on Modelsim that would run a program that is based off the Microprocessor with Interlocked Pipeline Stages (MIPS) instruction set. The processor will be 32 bits and will follow all of the properties of the original MIPS processor.

2. Literature Review

The main idea behind this project is to implement a basic MIPS processor ISA (Instruction Set Architecture) using Verilog. The literature associated and incorporated in this project is the five-stage pipelined data path which we learned in the Advanced Computer Architecture course. The organisational blocks that perform the major functions in this project are the Program Counter, Instruction Memory block, Register block, Arithmetic Logical Unit and the Data Memory block. Throughout this project we accommodate many more blocks like the Sign extend block, branching, Forwarding and Data Hazard blocks to prevent any Data and Control Hazards. A single cycle approach was taken initially to create a working MIPS implementation however, to reduce the implementation time and construct a more optimised architecture, the pipelines were introduced. So, through this project the pipelined implementation of the MIPS Instruction Set is designed and simulated.

3. Theoretical Background

With the pace and complexity of modern technology, it can become difficult and daunting to understand how a computer operates or comes to be. The first step in understanding and designing the modern computer is understanding its most critical component. The heart of a computer's operation is the processor. The computer processor is colloquially referred to as the brains of the computer. At its very simplest, all operations can be broken down from higher levels of abstraction to low machine level instructions. At its simplest, computers operate in binary but the language is difficult to understand. The first level of abstraction is found at the assembly level. The most commonly used assembly languages found in modern devices are ARM, x86, and MIPS, which is the focus of this lab.

 


Figure 3.1: R4700 Processor

The MIPS processor is a Reduced Instruction Set Computer (RISC) processor. The name refers to a processor and instruction set architecture that is simpler and efficient. The simpler processor design provides the advantage of abstraction, and in doing so, it favours productivity. The MIPS instruction set can be broken down into three instruction formats. The two most common types R-type and I-type instructions form the foundation of most assembly languages. The R-type instruction consists of a label and 3 operands, as shown in figure 3.1. The 32 bit instruction address can further be broken down in the format shown in figure 3.2.

add \$a0, \$s0, \$zero

Figure 3.2: R-Type Instruction

The first 6 bits provide us with the opcode. The opcode defines the general operation to be performed on the contents of the registers. The next 15 bits define the three addresses used in the R-type instruction. The source register is listed first, followed by the target register, and a destination register. After the register addresses, we have five bits that hold the shift amount (shamt) and the remaining six bits define the specific function performed. The I-type instruction possesses the same first 16 bits as the R-type instruction but the remaining 16 bits are used to define the address to which the read or write result should be written to.

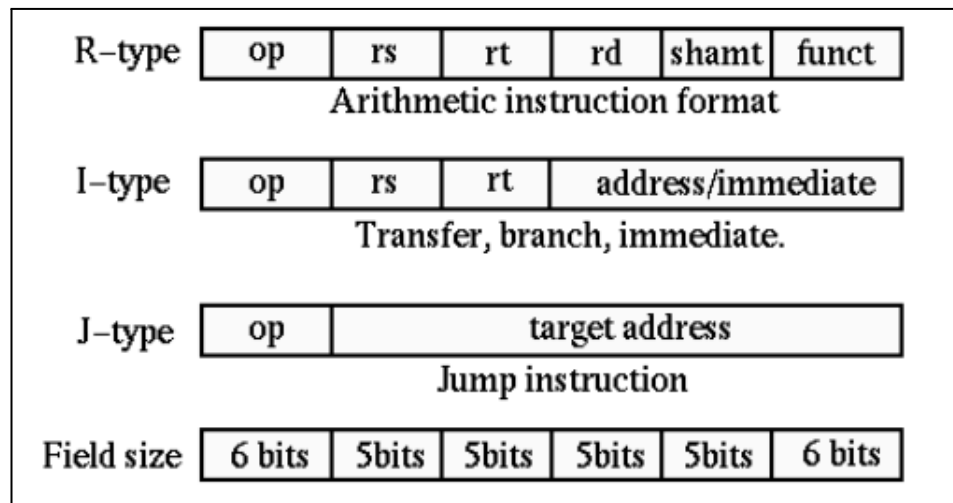


Figure 3.3: MIPS Instruction Format

The mips processor operates upon 32 registers where each register consists of four bytes. As shown in figure Table 3.1, the first instruction listed is the \$zero register and aptly named, for it holds a constant value of zero. The \$zero register is a prime example of the reserved registers that make up the 32 available registers. Among these reserved registers, we have the stack pointer \$sp and the return address \$ra, the latter of which is critical for recursive programming.

Table 3.1: MIPS Registers

| Name | Register Number | Purpose |
|-------------|-----------------|------------------------|
| \$zero | 0 | Constant 0 |
| \$at | 1 | Reserved for Compiler |
| \$v0 - \$v1 | 2 - 3 | Results |
| \$a0 - \$a3 | 4 - 7 | Arguments |
| \$t0 - \$t7 | 8 - 15 | Store temporary values |
| \$s0 - \$s7 | 16 - 23 | Store saved values |
| \$t8 - \$t9 | 24 - 25 | Store temporary values |
| \$k0 - \$k1 | 26 - 27 | Reserved for OS |
| \$gp | 28 | Global pointer |
| \$sp | 29 | Stack pointer |
| \$fp | 30 | Frame pointer |
| \$ra | 31 | Return Address |

Table 3.2: MIPS Instructions and OP Codes

| Operation | OP Code | Function Code |
|----------------------|---------|---------------|
| Add rd,rs,rt | 000000 | 100000 |
| Addi rt,rs,Immediate | 001000 | IMMEDIATE |
| Mult rs,rt | 000000 | 011000 |
| Div rs,rt | 000000 | 011010 |
| Nor rd,rs,rt | 000000 | 100111 |
| OR rd,rs,rt | 000000 | 100101 |
| AND rd,rs,rt | 000000 | 100100 |
| BEQ rs,rt,offset | 000100 | OFFSET |
| J target | 000010 | TARGET |
| SLT rd,rs,rt | 000000 | 101010 |
| MFHI | 000000 | 010000 |
| MFLO | 000000 | 010010 |
| Lw | 100011 | OFFSET |
| SW | 101011 | OFFSET |

As previously stated, the computer “thinks” or operates in the machine language binary. The binary language is implemented by hardware as voltage signals through circuit elements. Each individual signal or *Bit* travels on a single wire throughout the circuit with multiple bits moving along buses. The modules created in this project, such as the ALU and memory, are created through the use of combinational and sequential elements. The output of combinational circuits is dependent on the input composition. Sequential modules are dependent on the specific combination of inputs and the previous state of the machine. The sequential moniker alluding to the use of a clock to synchronise its operations to. With this in mind, we now possess the basic knowledge and components to build a single simple processor.

 


Figure 3.4: Pipelining Example

The Forwarding module is used in the Pipelined MIPS Datapath to reduce or even eliminate Data Hazards. In a Single Cycle MIPS datapath the value of an updated register is available only after the Memory Write back stage when the new value has been stored back into the register file. However, in pipelining, where multiple instructions are going through different stages of the pipeline simultaneously, then the updated value might be required before the Memory Writeback stage. In that case the Forwarding unit is used to ensure that the updated value of a register is passed onto the next instruction of the pipeline by forwarding the value straight after the execution stage and not waiting for the Memory Writeback to occur. This is how Forwarding is implemented.

4. Experimental Procedure

4.1 Instruction Stage Modules

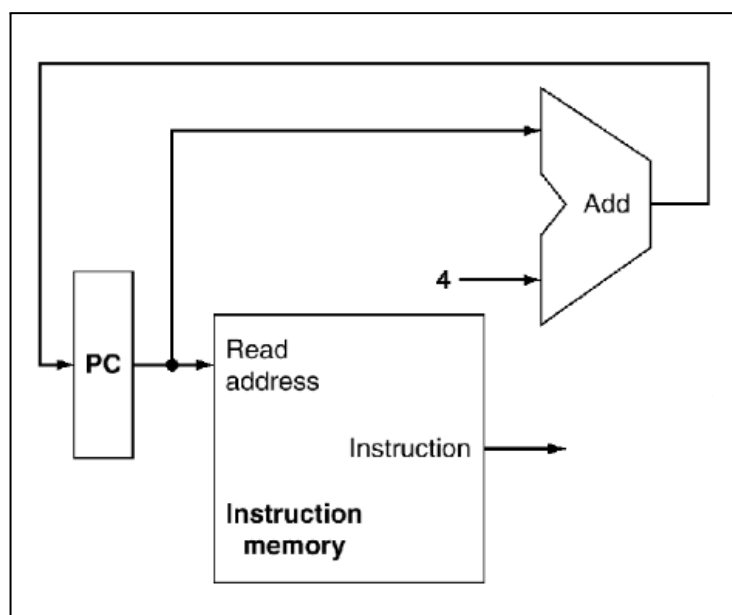


Figure 4.1: Instruction Stage Modules

MIPS instruction comprises various datapath elements connected together through wires and the first stage of the datapath includes the Instruction stage Modules, as can be seen in figure 4.1. This stage of the datapath includes the Program Counter, Instruction Memory and an Adder. The program counter is responsible for holding the address of the current instruction. In this stage the PC is also responsible for holding the address of the next instruction being input upon its incrementation from the Adder. The Program counter then forwards the instruction to the Instruction memory which, like the name suggests, stores the instruction in it for it to be decoded in the Instruction Fetch/Instruction Decode (IF/ID) pipeline register (Figure 4.6). So, overall this stage performs fetching and storing of the instruction.

4.2 Control Module

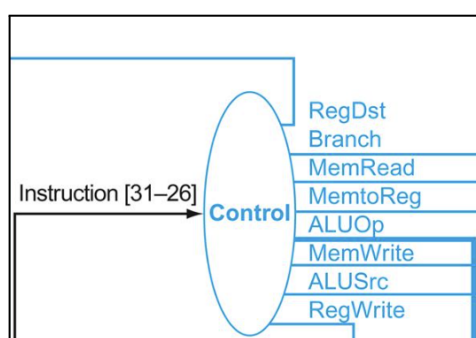


Figure 4.2: Control Module

The functionality of the pipelined datapath is determined by the Control Module (Figure 4.2). The Instruction OpCode is passed as an input to the control module and according to the OpCode the Control module decides which function will be carried out. The Control module has various signal outputs (Figure 4.5) which act as the signal inputs to all the datapath modules.

RegDst - The RegDst signal determines if the Destination register is specified as the Rd or the Rt register in the case of an R or an I type instruction.

Branch - The Branch signal goes into a mux to decide whether the instruction will branch off to another instruction or not. This functionality will be used in the case of beq (Branch on Equal) instruction.

MemRead - The MemRead signal enables memory to be read from the Data Memory in the case of Load instruction.

MemtoReg - The MemtoReg signal decides if the ALU Output or the Data Memory output value will be written back to the register file.

ALUOp - The ALUOp signal is a 2 bit signal that decides which operation will be executed in the ALU by passing 2 bits to the ALU Control module.

MemWrite - The MemWrite signal enables memory to be written to the Data memory in the case of Store instruction.

ALUSrc - The ALUSrc signal decides which operand from the Rt or the Rd will be passed to the ALU as the second source operand. This signal is only used in the Single Cycle Implementation and gets replaced by the Forwarding unit signals for the pipelined datapath.

RegWrite - The RegWrite signal enables the final output to be written to the Register File. Every module receives its signal values which are generated by the Control module depending on the OpCode.

4.3 Register File

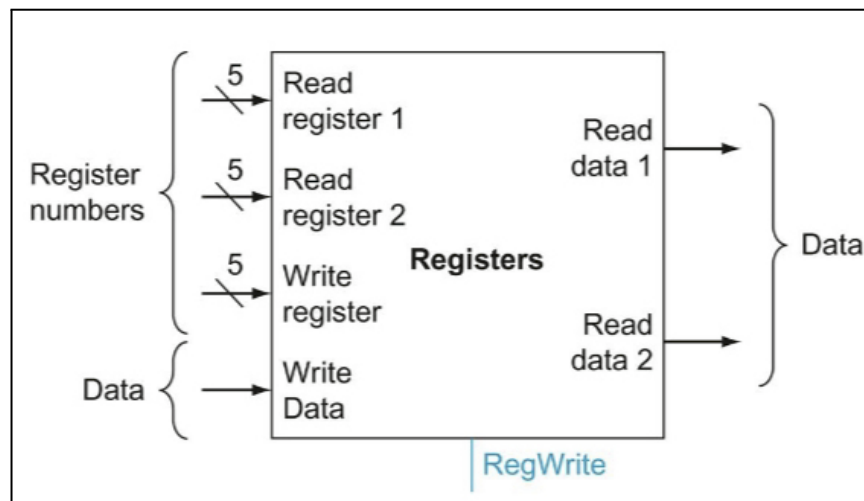


Figure 4.3: Register File

The output from the Instruction memory is decoded by using the first pipelining stage, Instruction Fetch and Instruction Decode (Figure 4.6). The IF/ID stage fetches the 32 bit instruction from the instruction memory and decodes it into different outputs based on the type of function and the Field size associated with each function, as seen in Figure 3.2. The decoded instruction is passed onto the register file which consists of various registers within it (Figure 4.3). The Read register 1 and Read register 2 are the two registers which read the 2 decoded data words in the case of an R or I type instruction. These 2 registers get 5 bit inputs each into them to specify one of the 32 registers ($2^5=32$) and the 2 output buses, namely Read data 1 and Read data 2, output the data in those registers to the following stages. The final output is also written back into the register file and for that purpose we have the Write register which stores the address for the register the data will be written back to and the Write Data has the actual output data in it that needs to be stored.

4.4 Forwarding Unit

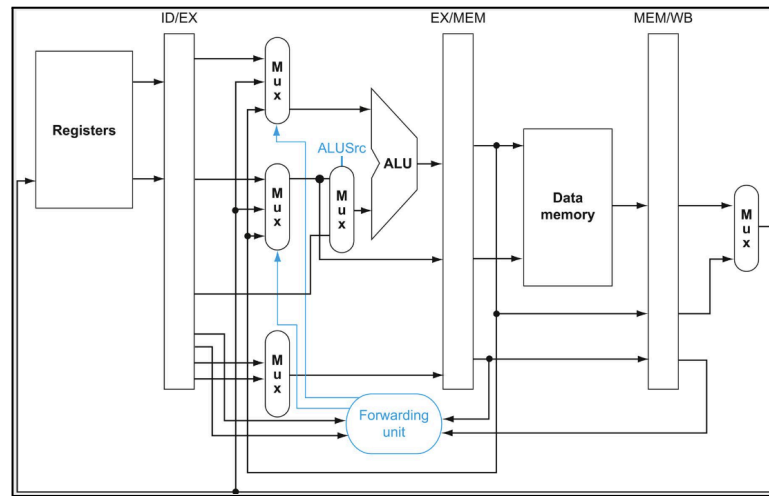


Figure 4.4: Forwarding Unit

The Forwarding unit is useful to avoid Data Hazards by forwarding the updated register values right after the Execution stage to the next instruction. It ensures that the Execution stage of the next instruction gets the updated values of the registers in it. The Forwarding module checks for an EX/MEM data hazard if the current instruction in its Execution stage has a previous instruction that will write to the register file and the destination of that instruction is one of the source registers that is in its Execution stage. To resolve it the forwarding unit sends the ForwardA signal to the Multiplexer which forwards the correct value from the EX/MEM register to the ALU's first input. Another hazard that the forwarding can resolve is the MEM/WB hazard. For this purpose the Forwarding module detects the same hazard but between the MEM/WB and the register value going into the Execution stage. To resolve this hazard the forwarding module sends the ForwardB signal to the Multiplexer which forwards the correct value from the MEM/WB register to the ALU's second input.

The outputs from the 2 data output buses are passed onto the ID/EX pipeline register which holds these 2 values as well as the target address in the case of a branch instruction. The target address is 16 bits and it passes through a sign extension unit to create a 32 bit address for the branching. So overall these 3 register values are passed onto the ID/EX register which holds onto them before passing them to the ALU.

The Arithmetic Logic Unit or ALU (Figure 4.5) is the next stage in the datapath where all the computations of all the instructions are executed. The ALU has the following instructions that are being implemented in it :

- Arithmetic/ logic operations : and, or, nor, add, sub, slt, addi, div, mult
- Data movement operations : lw, sw, mfhi, mflo
- Flow control operations : beq, j

All of these operations have their Operation Code and Function Code which is tabulated in Table 3.2. Out of all these operations the ALU chooses which operation to perform according to the ALU Operation Signal (Table 3.2) coming in from the Control Module. This signal decides which operation is to be executed on the register operands and the result of the operation is passed out onto the next stage of the pipeline.

4.7 Data Memory

 


Figure 4.7: Data Memory

The ALU output is passed onto the EX/MEM pipeline register which again acts as a buffer similar to the other pipeline registers. This register holds the ALU output before passing it onto the Data memory module.

The Data Memory module is the other storage module which is used in the case of load word or store word instructions (Figure 4.6). The ALU output is stored in the Address input of the module since the load and store operations require an address to load from or store to. Using the MemWrite and MemRead control inputs, the Data Memory module decides whether to load a value from the memory using the Read Data output and send it back to the Register File for storing that value, or store data in memory using the Write Data input. In the case of an R type instruction there is no use of the Data Memory so this stage is skipped in that case as it can be seen in Figure 4.7.

The output from the Data Memory is passed into the MEM/WB pipeline register which acts as a storage register or a buffer in case of hazards. The MEM/WB register holds the output coming from the Data Memory in case of load instruction or the ALU output in the case of an R type instruction. The pipeline register then passes the stored values back to the Register file for storing.

4.8 Single Cycle Implementation

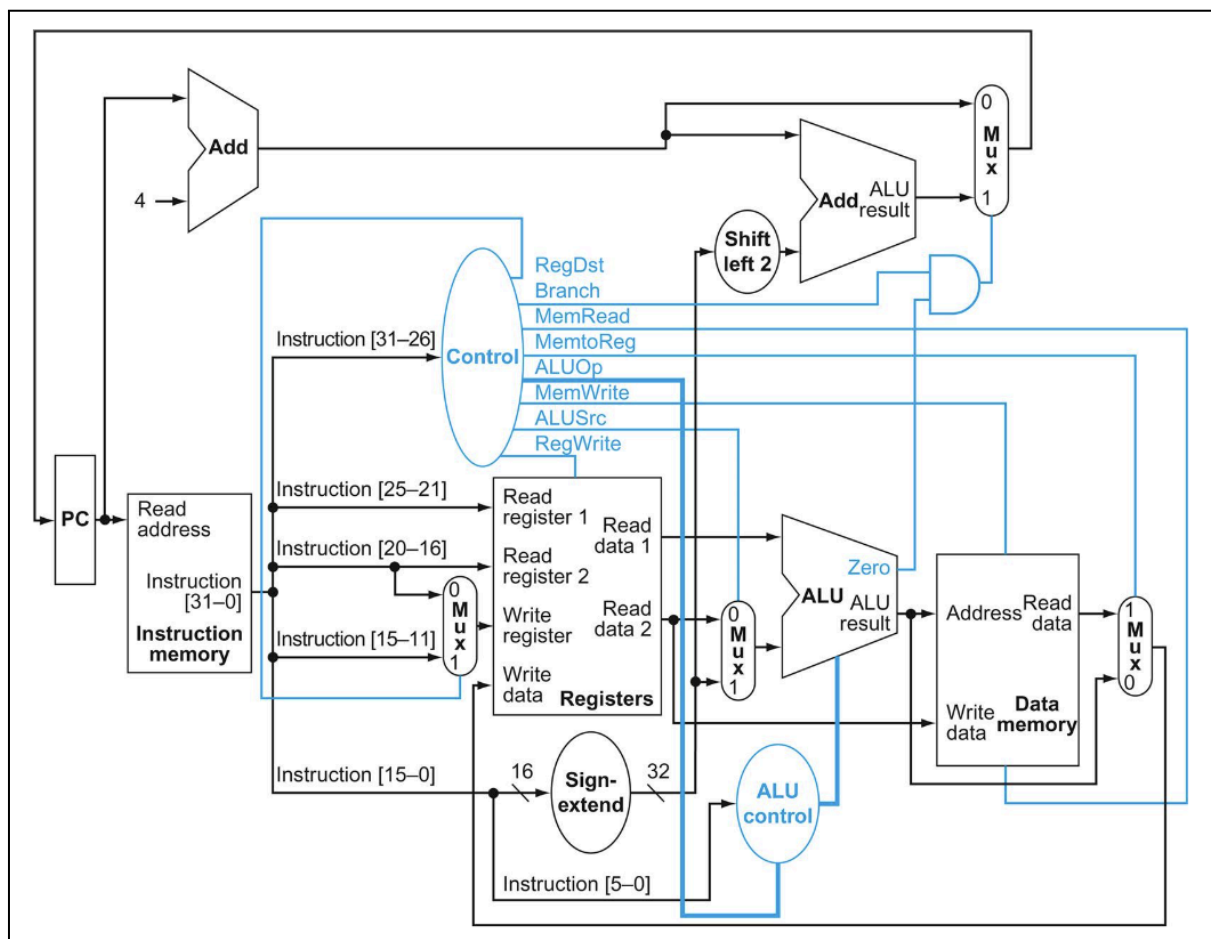


Figure 4.8: Single Cycle MIPS Datapath

Upon combining all of the above mentioned modules without the pipeline stages, we get the Single Cycle MIPS datapath (Figure 4.8). This datapath shows the complete flow of data from the program counter to the Final Data Memory with all the wires showing the port connections between each module. For this purpose a separate module was created called the Top Module (Appendix Z) which connected all of the modules shown in Figure 4.8 to make a single module.

4.9 Pipeline Registers

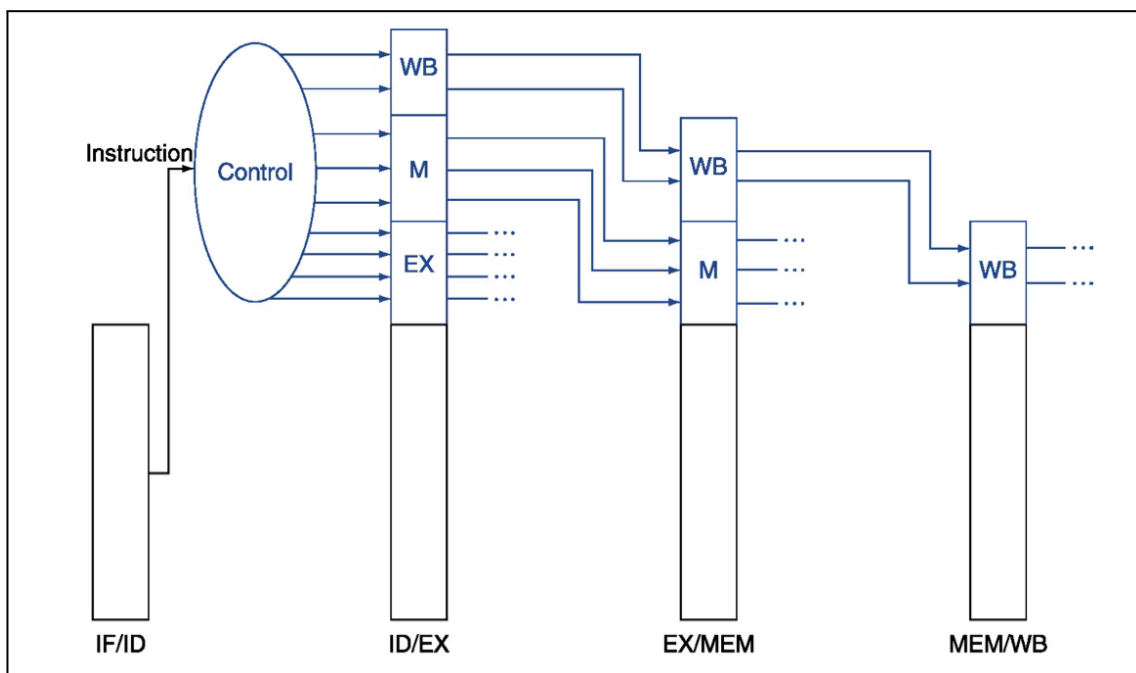


Figure 4.9: Pipeline Registers

All the pipeline stages that are used for the MIPS Implementation can be seen in Figure 4.9. The IF/ID pipeline is used to store the Instruction coming in from the Program Counter and then decode it according to the operation followed by the passing of the first 6 bits to the Control module and the rest to the register module depending on the Instruction to be executed.

The ID/EX pipeline module gets the outputs from the Register File along with the control module signals and holds those values before passing them onto the ALU module through multiplexers and to the Forwarding module for hazard resolution.

The EX/MEM pipeline module holds the outputs coming from the ALU and passes them onto the Data Memory module in the case of a load or store operation, or passes the ALU output to the MEM/WB pipeline register in the case of a R type instruction.

The MEM/WB pipeline module holds the output from the Data Memory in the case of a Load instruction or the ALU output in the case of a R type instruction, and passes the value onto the Register file for storing.

4.10 Pipelined Implementation (Top Module)

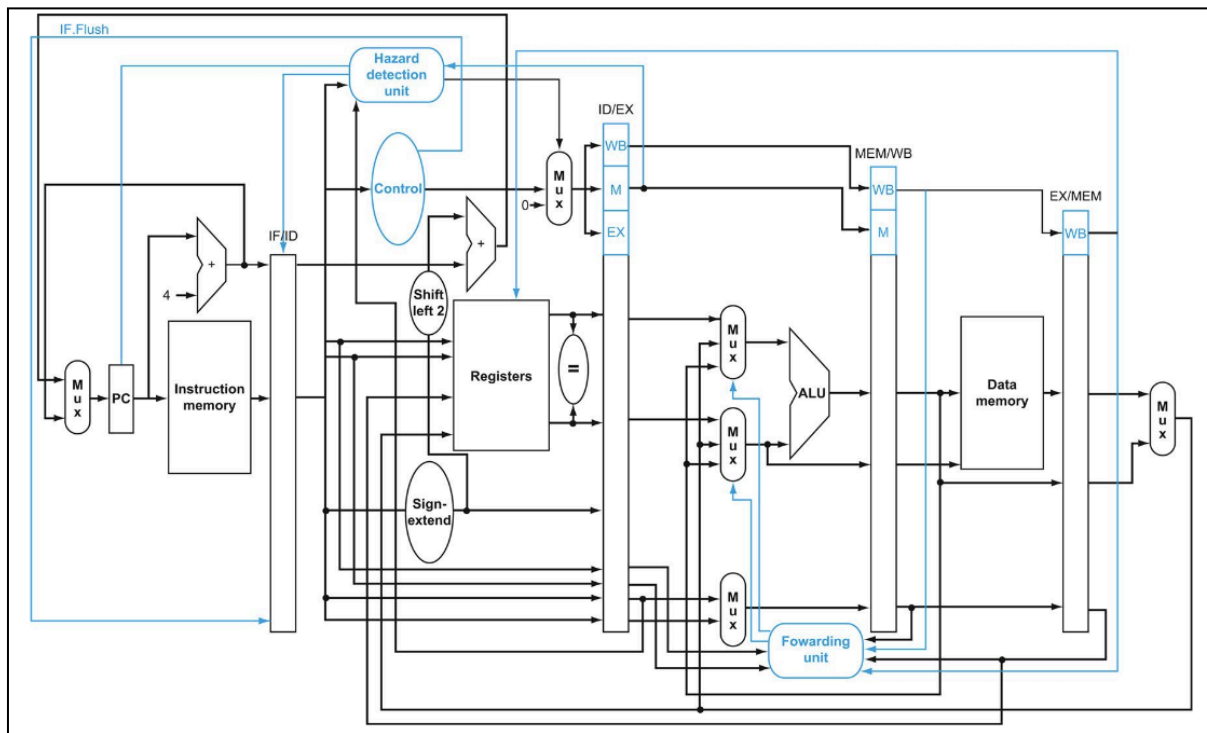


Figure 4.10: MIPS Pipelined Datapath

After the implementation of all the modules along with the pipelines, we get the final pipelined datapath as it can be seen in Figure 4.10. This final datapath has all the modules connected together using wires which were incorporated using a Top Level Module. All the modules are connected using ports and instantiations in the Top Level module (Appendix Z), and then finally, all the 3 types of instructions can be synthesised and simulated on this MIPS architecture design model.

4.11 Equipment Used

| Equipment Used | Description |
|----------------|---|
| Quartus | High level hardware development and synthesis IDE |
| ModelSim | High level hardware development software |
| PC | Personal computer used for coding |
| DE2-115 | FPGA development kit |

To test the operation of the ALU's AND operation, the instruction h'00E80824 is passed from the instruction memory to the IF/ID stage pipeline. Here the instruction is decoded to an add instruction that will use values of \$T7 and \$T8 located at address h'0111 and h'1000 respectively. When the values of b'1101 and b'0100 are and together, we get a final 32 bit value of b'0100. Figure 5.12 shows that the result of the AND operation are indeed written to the register specified in the hex instruction which results in the value written to \$V1 located at address h'0001.

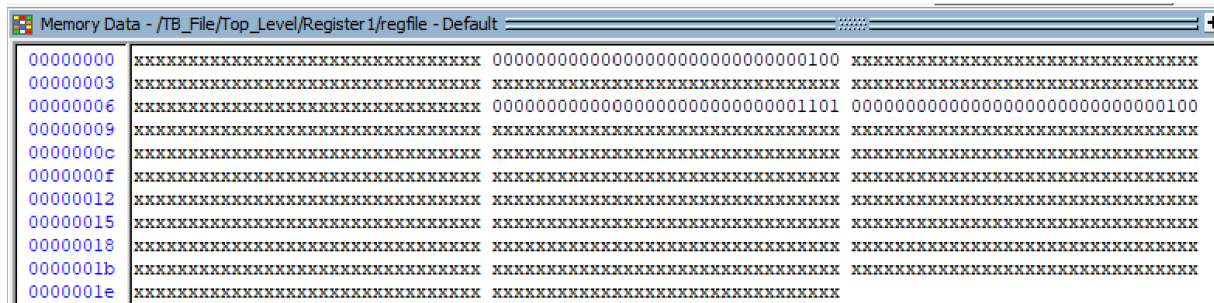


Figure 5.12: Results of AND Operation Written To Destination Register

5.6 Nor Simulation Results

 


Figure 5.13: Register Contents Prior to Simulation of NOR Operation

Similar to the previous operation, the instruction `h'01070827` specifies a `nor` operation that will take the values located at addresses `h'0110` and `h'0111`. The variable `$T6` has a binary value of `b'1010` and variable `$T7` is initialised to the value `b'0001`, shown in figure 5.13. When we `nor` these values together, we expect to see the 32 bit value `b'11111111111111111111111111110100` stored in the destination register located at address `h'0001`, which is labelled as `$V1`. After five Clock cycles, we can see that the expected value was written to the correct address confirming the operation of the ALU's NOR calculation.

The Final waveform for an Add operation was displayed as it can be seen in Figure 5.21. The Hex code 0x00E80820 is passed to the Instruction Memory and the complete implementation of each stage of the Top Module is allowed to execute. As a result, the complete waveform of a fully working Add operation using MIPS Architecture can be observed in Figure 5.21.

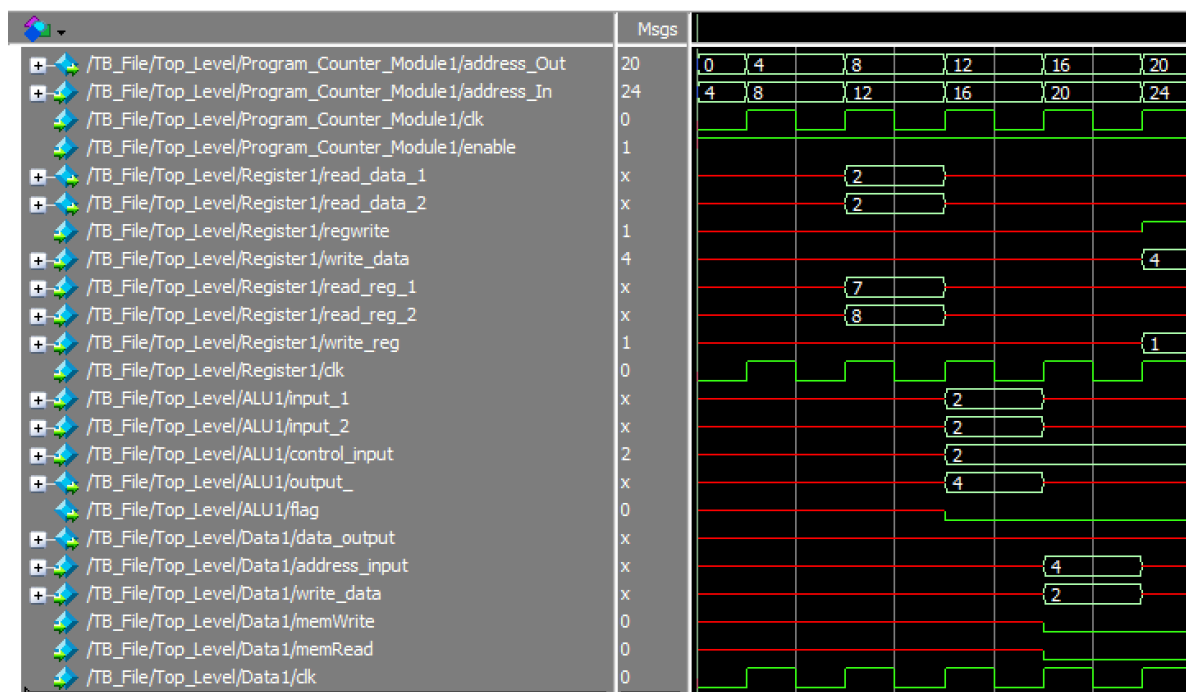


Figure 5.21: Complete Waveform for Add Operation

Registers \$7 and \$8 were initialised with the value 2 as it can be seen in the second high clock signal and these 2 registers are the source register that are passed on as inputs to the ALU module. The ALU module performs Addition function on the values in these registers i.e. it adds 2 stored in \$7 to the 2 stored in \$8, to give the ALU output as 4. This output is then passed onto the register file where it gets stored back in Register \$1.

5.10 Multiplication Simulation Results


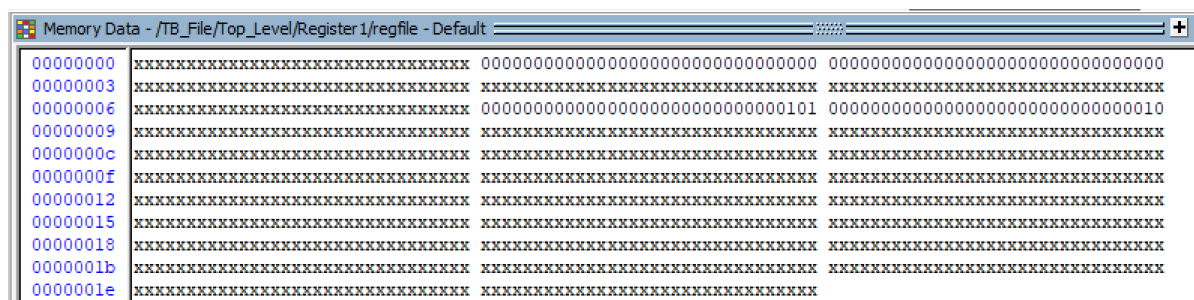


Figure 5.22: Register File Prior to Multiplication

Figure 5.22 shows the contents of the register file initialised with the values d'5 held at address b'00111 and integer value d'2 stored at register address b'01000. In order to perform the multiplication instruction, the hex instruction code of h'01070018 was passed from instruction memory to the IF/ID pipeline register. Once decoded we see that we are multiplying the values held in \$T7 and \$T8. The result of this multiplication will not be stored to a destination register but stored with the Hi and Lo registers within the ALU module.

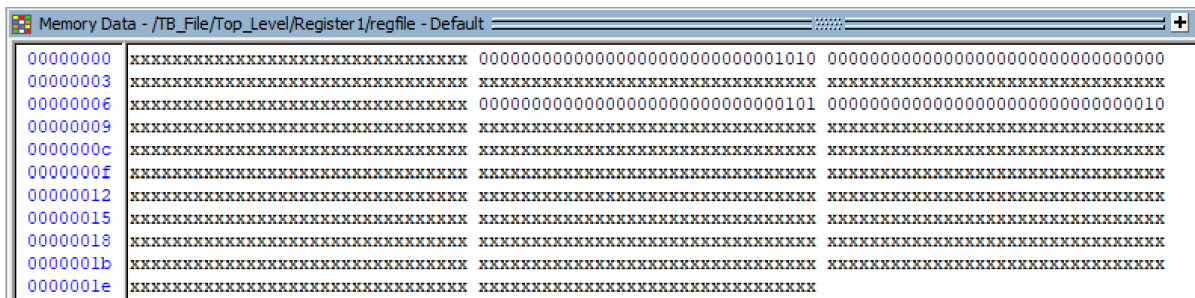

Since we are storing the values in the HI and LO registers, we require another instruction to move the values out of the HI/LO ALU registers. As shown in figure 5.24, after 3 clock cycles the value d'10 is stored in the LO register. Then when the PC counter increments to the next instruction, we get the instruction h'00000812 is passed into the pipeline. This instruction breaks down to a move from lo (MFLO) operation that will take the 32 bit value held in the ALU Lo register and store it in the address b'00001.

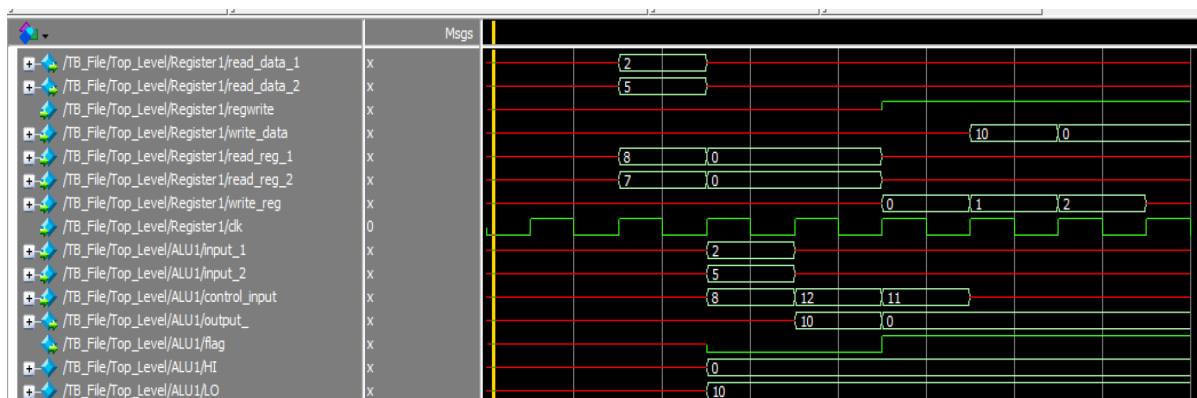


Figure 5.24: Multiplication Waveform

Furthermore, the next instruction to enter the pipeline is h'0000101 which translates to a move from high (MFHI) operation that will store the value stored in the high register and moves it to the destination register b'00010. Shown in figure 5.23, we see that the low value d'10 is indeed stored at address b'00001 the destination register of \$V1 and the high value of d'0 is stored at address b'00010 which is the result register of \$V2.

5.11 Division Simulation Results

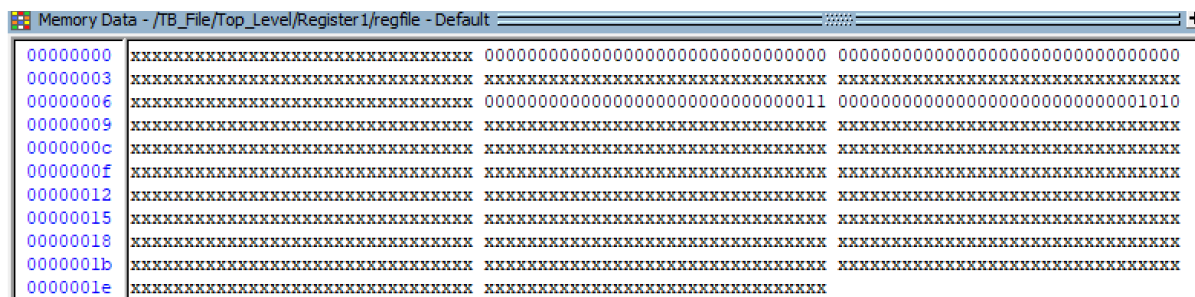


Figure 5.25: Registers Initialised Prior to Division Operation

The division instruction comes into the pipeline with the value h'0107001A. This instruction will be broken down into a division operation that will divide the integer value d'3 stored at address location b'00111 and the value d'10 stored at register address b'01000

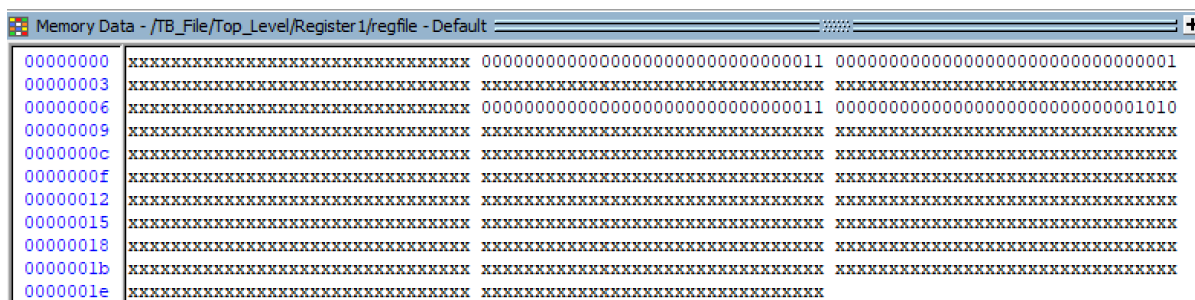


Figure 5.26: Register Contents Post Division

As we can see in figure 5.26, as we can see the value stored in address b'00001 is d'3 which is the result we expect when dividing 10 by 3 and the remainder of d'1 is stored at register b'00010. The values stored in these registers come from the high and lo registers as shown in figure 5.27.

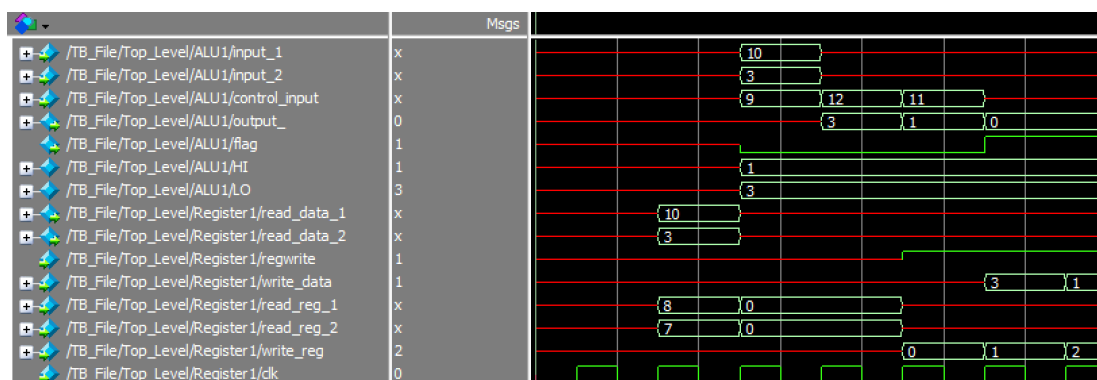


Figure 5.27: High and Low Register Waveforms

5.12 Forwarding Unit Simulation Results

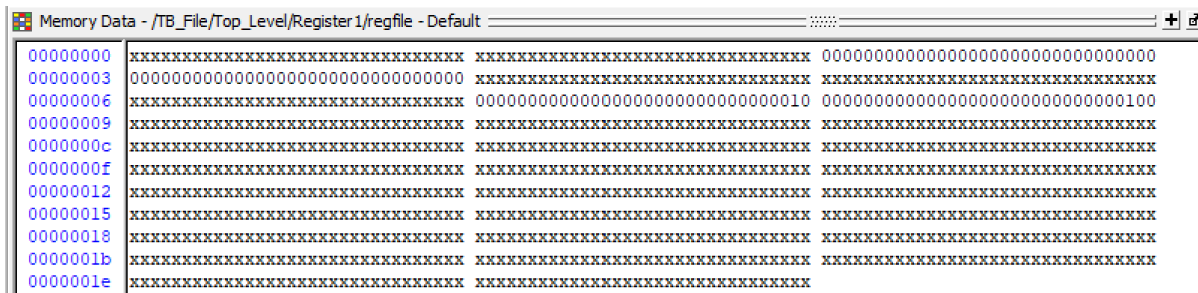


Figure 5.28: Register Module Before Forwarding

In order to test the forwarding, we placed instructions in the instruction memory. The first instruction will store the values held in registers \$T7 and \$T8 and store the value in register \$T2. If the forwarding operated as expected we should see a value of d'6 written to register \$T3

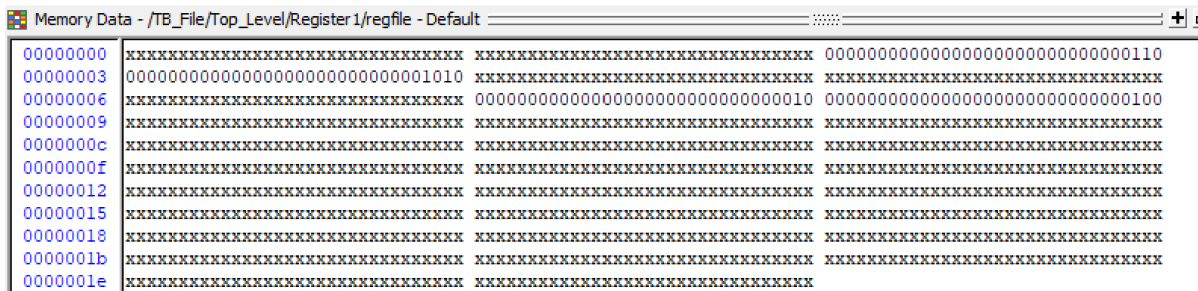


Figure 5.29: Register Contents After Forwarding

As shown in figure 5.29, we indeed stored the value d'6 into register \$T3 located at address b'00110. In the figure below, we see the forward unit check whether the next instruction in the pipeline requires data that has not yet been returned. In figure 5.30, we see that the forwarding unit detects the need to forward and forwards it to the next instruction.

 


Figure 5.30: Forwarding Unit Waveform

5.13 Hazard Unit Simulation Results

| Address | Data | ... |
|----------|----------------------------------|----------------------------------|
| 00000000 | 00000000000000000000000000000000 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000003 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000006 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | 00000000000000000000000000000000 |
| 00000009 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000000c | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000000f | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000012 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000015 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000018 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000001b | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000001e | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |

Figure 5.31: Register Module Before Hazarding

In order to test the hazard unit, we placed a load instruction into the pipeline of h'8C080000 and a following instruction of h'00E80820. This will create a load data hazard because the first instruction is a load instruction that is loading the value stored at address b'00000 to variable \$T8 located at address b'01000. The instruction following the load is a simple add instruction.

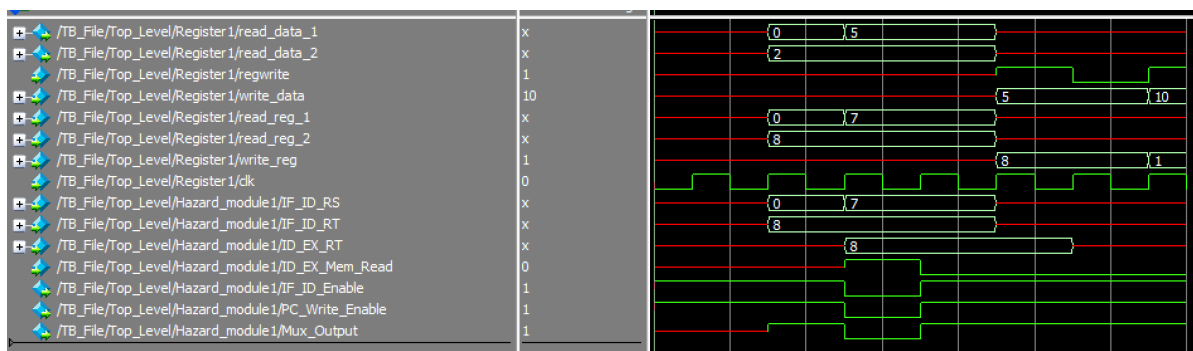


Figure 5.32: Hazard Unit Detection in Waveform

This instruction requires the use of the value held in variable \$T8. As shown in the, in figure 5.32, we are detecting a need to handle a hazard and the pc write enable goes to zero to introduce a bubble into the pipeline. Figure 5.33 shows that the correct value was stored in register address b'01000 of d'5.

| Address | Data | ... |
|----------|----------------------------------|----------------------------------|
| 00000000 | 00000000000000000000000000000000 | 00000000000000000000000000000000 |
| 00000003 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000006 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | 00000000000000000000000000000000 |
| 00000009 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000000c | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000000f | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000012 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000015 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 00000018 | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000001b | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |
| 0000001e | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx | xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx |

Figure 5.33: Register Module After Hazard Detection

5.14 Branch If Equal Simulation Results

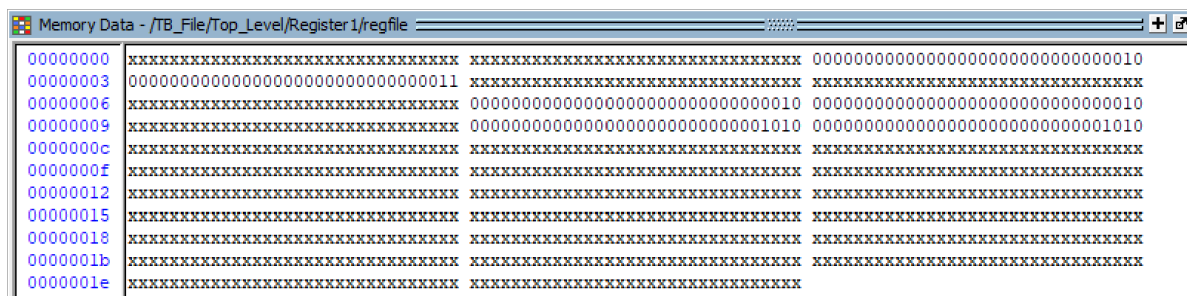


Figure 5.35: Register Module Before Branch Instruction

In order to test if our branch if equal instruction is functioning correctly, we placed two instructions following the branch check. The contents of \$t10 at address b'01010 and \$t11 stored at b'1011. Since the values held there are correct, we will skip the and instruction in our pipeline and instead we will jump to instruction 12 which will perform a subtraction on the contents of address \$T7 and \$T8 and store it in to register \$t3.

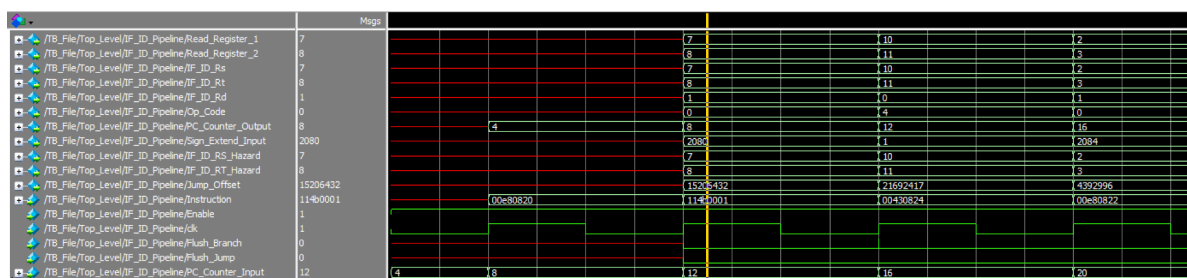


Figure 5.36: Branch If Equal Waveform

When we observe the waveform shown in figure 5.36, we see that the address is updated from the next instruction to the one after that one and the flush signal goes to zero indicating that a branch instruction did occur.


5.15 Jump Instruction Simulation Results



Figure 5.38: Jump Instruction Waveform

The hex instruction detailing a jump is the hex value h'80000003. We can see from the waveform in figure 5.38, we see that flush jump has gone high and the flush branch goes low. This indicates that our jump is performing as expected.

5.16 Synthesization Results

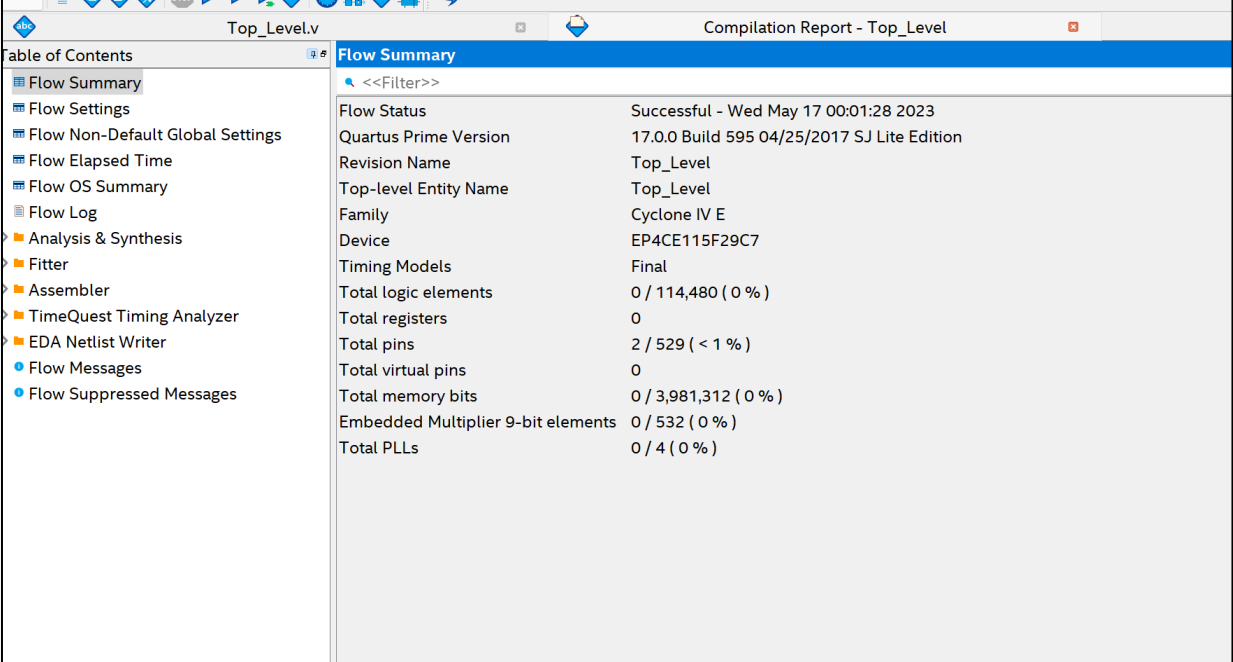

| Flow Summary | |
|------------------------------------|---|
| <<Filter>> | |
| Flow Status | Successful - Wed May 17 00:01:28 2023 |
| Quartus Prime Version | 17.0.0 Build 595 04/25/2017 SJ Lite Edition |
| Revision Name | Top_Level |
| Top-level Entity Name | Top_Level |
| Family | Cyclone IV E |
| Device | EP4CE115F29C7 |
| Timing Models | Final |
| Total logic elements | 0 / 114,480 (0 %) |
| Total registers | 0 |
| Total pins | 2 / 529 (< 1 %) |
| Total virtual pins | 0 |
| Total memory bits | 0 / 3,981,312 (0 %) |
| Embedded Multiplier 9-bit elements | 0 / 532 (0 %) |
| Total PLLs | 0 / 4 (0 %) |

Figure 5.39: Synthesization Results

The synthesization results were unexpected. We had previously synthesised our project with block ram appearing in this report but as shown in figure 5.39, we must have produced an error that caused the block ram to stop synthesising.

6. Conclusion

Through this project we were able to design and implement a processor on Modelsim that would run a program that is based off the Microprocessor with Interlocked Pipeline Stages (MIPS) instruction to perform Arithmetic/Logic, Data Movement and Flow Control instructions depending on the instruction passed in by the user. For the design we implemented a 5 stage pipelined datapath to improve execution time and included hazard detection and Forwarding units to avoid Data and Control hazards. The complete pipelined cycle can be seen in Figure 4.10 and it was constructed through Verilog coded modules for each stage of the instruction and a Top Module connecting all the modules together for a complete cycle was also constructed. As a result the complete waveform (Figure 5.21) of a fully operational MIPS ISA was fabricated.

7. References

Patterson, David, A. and John L. Hennessy. Computer Organization and Design MIPS Edition. Available from: California State University - Fresno, (6th Edition). Elsevier S & T, 2020.

8. Appendices

Appendix A

```
module Adder_32_bit(input [31:0] a,b,output reg [31:0] out);
always@(a,b)
begin
    out = a + b;
end
Endmodule
```


Appendix B

```

module ALU_Module(input_1, input_2, output_, control_input, flag);
input [31:0] input_1, input_2;
input [3:0] control_input;
output reg [31:0] output_;
output reg flag;
reg [31:0] HI, LO;
always@( input_1, input_2, control_input)
begin
case(control_input)
0 :
    output_ = input_1 & input_2;
1:
output_ = input_1 | input_2;
2: output_ = input_1 + input_2;
6: output_ = input_1 - input_2;
7 : output_ = (input_1 < input_2 ? 1 : 0);
8:
    begin
    {HI, LO} = input_1 * input_2;
    end
9:
    begin
    if( ~(input_2 == 32'd0) )
    begin
    HI = input_1 % input_2;
    LO = input_1 / input_2;
    end
    end
10 : output_ = ~(input_1 | input_2);
11: output_ = HI;
12: output_ = LO;
default : output_ = 0;

endcase

if (output_ == 0)
begin
    flag = 1;
end
else
begin
    flag = 0;
end

end
endmodule

```

Appendix C

```

module ALU_Module(input_1, input_2, output_, control_input, flag);

input [31:0] input_1, input_2;
input [3:0] control_input;

output reg [31:0] output_;
output reg flag;

reg [31:0] HI, LO;

always@( input_1, input_2, control_input)

begin

case(control_input)

0 :
    output_ = input_1 & input_2;
1:
    output_ = input_1 | input_2;
2: output_ = input_1 + input_2;
6: output_ = input_1 - input_2;
7 : output_ = (input_1 < input_2 ? 1 : 0);
8:
    begin

        {HI, LO} = input_1 * input_2;

    end

9:
    begin
        if( ~(input_2 == 32'd0) )
        begin
            HI = input_1 % input_2;
            LO = input_1 / input_2;
        end
    end
10 : output_ = ~(input_1 | input_2);

11: output_ = HI;

12: output_ = LO;
default : output_ = 0;

```

```
endcase

if (output_ == 0)
    begin
        flag = 1;
    end
else
    begin
        flag = 0;
    end
end

end

Endmodule
```

Appendix D

```
module AND_Gate(output out , input a ,b);  
always@(*)begin  
out = a &b;  
end  
endmodule
```

Appendix E

```
module Comparator( out , a , b);  
output reg out;  
input [31:0] a , b;  
always@(*)begin  
    if( a == b)  
        begin  
            out = 1;  
        end  
    else  
        begin  
            out = 0;  
        end  
end  
endmodule
```

Appendix F

```
module Concatenation_28_32(out, a , b);  
output reg [31:0] out;  
input [27:0] a;  
input [31:0] b;  
always@(*)  
begin  
    out[31: 28] = b [31: 28];  
    out [27:0]  = a ;  
end  
endmodule
```

Appendix G

```

module Data_Memory_Module(
    output reg [31:0] data_output,
    input [31:0] address_input,
    input [31:0] write_data,
    input memWrite,
    input memRead,
    input clk
);

    reg [31:0] memfile[0:31];
initial
begin
    memfile [32'd0] = 32'd10;
end
always@(negedge clk)
    begin
        if (memWrite == 1)
            begin
                memfile[address_input] = write_data;
            end
        end
    end
always@(negedge clk)
    begin
        if( memRead == 1)
            begin
                data_output = memfile[address_input];
            end
        end
    end
endmodule

```

Appendix H

```

module EX_MEM_Pipeline_Module (
output reg RegWrite_Output, MemtoReg_Output, MemRead_Output, MemWrite_Output,
output reg [4:0] EX_MEM_RD_Fowarding, EX_MEM_RD_Next_Pipeline,
output reg [31:0] ALU_Result_Output,
output reg [31:0] RT_32_Bit_Output,
input RegWrite_Input, MemtoReg_Input, MemRead_Input, MemWrite_Input,
input [4:0] ID_EX_MUX,
input [31:0] ALU_Result_Input,
input [31:0] RT_32_Bit_Input,
input clk
);
always@(posedge clk)begin
    RegWrite_Output = RegWrite_Input;
    MemtoReg_Output = MemtoReg_Input;
    MemRead_Output = MemRead_Input;
    MemWrite_Output = MemWrite_Input;
    EX_MEM_RD_Fowarding = ID_EX_MUX;
    EX_MEM_RD_Next_Pipeline = ID_EX_MUX;
    ALU_Result_Output = ALU_Result_Input;
    RT_32_Bit_Output = RT_32_Bit_Input;
end
endmodule

```


Appendix I

```

module Forward_Unit_Module(forward_A ,forward_B, ID_EX_RS, ID_EX_RT, EX_MEM_RD ,
MEM_WB_RD, EX_MEM_Reg_Write, MEM_WB_Reg_Write);
input [4:0] ID_EX_RS, ID_EX_RT , EX_MEM_RD, MEM_WB_RD;
input EX_MEM_Reg_Write, MEM_WB_Reg_Write;
output reg [1:0] forward_A, forward_B;
always@(ID_EX_RS, EX_MEM_RD, MEM_WB_RD)
begin
    if( ((ID_EX_RS == EX_MEM_RD) & (EX_MEM_Reg_Write == 1))| ((ID_EX_RS ==
EX_MEM_RD)& (ID_EX_RS == MEM_WB_RD) & (EX_MEM_Reg_Write == 1)) )
        begin
            forward_A = 2'b10;
        end
    else if( (ID_EX_RS == MEM_WB_RD) & (MEM_WB_Reg_Write == 1) )
        begin
            forward_A = 2'b01;
        end
    else
        forward_A = 2'b00;
    end
always@(ID_EX_RT, EX_MEM_RD , MEM_WB_RD)
begin
    if( ((ID_EX_RT == EX_MEM_RD) & (EX_MEM_Reg_Write == 1))| (
(ID_EX_RT==EX_MEM_RD) & (ID_EX_RT == MEM_WB_RD) & (EX_MEM_Reg_Write == 1)
))
        begin
            forward_B = 2'b10;
        end
    else if( (ID_EX_RT == MEM_WB_RD) & (MEM_WB_Reg_Write == 1))
        begin
            forward_B = 2'b01;
        end
    else
        forward_B = 2'b00;
    end
end
endmodule

```

Appendix J

```

module Hazard_Unit_Module (PC_Write_Enable, IF_ID_Enable, Mux_Output, ID_EX_Mem_Read ,
IF_ID_RS, IF_ID_RT, ID_EX_RT);
input [4:0] IF_ID_RS, IF_ID_RT, ID_EX_RT;
input ID_EX_Mem_Read;
output reg IF_ID_Enable;
output reg PC_Write_Enable;
output reg Mux_Output;

initial
begin
    IF_ID_Enable = 1;
    PC_Write_Enable = 1;
end

always@(*)
begin
    if( ( (ID_EX_Mem_Read==1) & ((ID_EX_RT == IF_ID_RT) | (ID_EX_RT == IF_ID_RS) )
    ) )
        begin
            Mux_Output = 0;
            IF_ID_Enable = 0;
            PC_Write_Enable = 0;
        end
    else
        begin
            Mux_Output = 1;
            IF_ID_Enable = 1;
            PC_Write_Enable = 1;
        end
    end
end
endmodule

```

Appendix K

```

module ID_EX_Pipeline_Module(ALU_Src_Out, Regwrite_Output, MemtoReg_Output,
MemRead_Output, MemWrite_Output, RegDst_Output, ALUOp_Output, Sign_Extend_Output,
ID_EX_Rs_Fowarding, ID_EX_Rt_Fowarding, ID_EX_Rt_MUX, ID_EX_Rd_MUX,
Read_Data_1_Output, Read_Data_2_Output, Regwrite_Input, MemtoReg_Input, MemRead_Input,
MemWrite_Input, RegDst_Input, ALUOp_Input, Sign_Extend_Input, IF_ID_Rs,
IF_ID_Rt, IF_ID_Rd, Read_Data_1_Input, Read_Data_2_Input, clk, ALU_Src_In);
output reg Regwrite_Output, MemtoReg_Output, MemRead_Output, MemWrite_Output,
RegDst_Output, ALU_Src_Out;
output reg [1:0] ALUOp_Output;
output reg [31:0] Sign_Extend_Output;
output reg [4:0] ID_EX_Rs_Fowarding, ID_EX_Rt_Fowarding,
ID_EX_Rt_MUX, ID_EX_Rd_MUX;
output reg [31:0] Read_Data_1_Output, Read_Data_2_Output;
input Regwrite_Input, MemtoReg_Input, MemRead_Input, MemWrite_Input, RegDst_Input,
ALU_Src_In;
input [1:0] ALUOp_Input;
input [31:0] Sign_Extend_Input;
input [4:0] IF_ID_Rs, IF_ID_Rt, IF_ID_Rd;
input [31:0] Read_Data_1_Input, Read_Data_2_Input;
input clk;

always@(posedge clk)begin
    Regwrite_Output = Regwrite_Input;
    MemtoReg_Output = MemtoReg_Input;
    MemRead_Output = MemRead_Input;
    MemWrite_Output = MemWrite_Input;
    RegDst_Output = RegDst_Input;
    ALUOp_Output = ALUOp_Input;
    Sign_Extend_Output = Sign_Extend_Input;
    ID_EX_Rs_Fowarding = IF_ID_Rs;
    ID_EX_Rt_Fowarding = IF_ID_Rt;
    ID_EX_Rt_MUX = IF_ID_Rt;
    ID_EX_Rd_MUX = IF_ID_Rd;
    Read_Data_1_Output = Read_Data_1_Input;
    Read_Data_2_Output = Read_Data_2_Input;
    ALU_Src_Out = ALU_Src_In;
end
endmodule

```

Appendix L

```

module IF_ID_Pipeline_Module(Jump_Offset, IF_ID_RS_Hazard, IF_ID_RT_Hazard,
PC_Counter_Output, Op_Code, Read_Register_1, Read_Register_2, IF_ID_Rs, IF_ID_Rt,
IF_ID_Rd ,Sign_Extend_Input, Enable, Instruction, clk, PC_Counter_Input, Flush_Jump,
Flush_Branch);
output reg [4:0] Read_Register_1, Read_Register_2, IF_ID_Rs, IF_ID_Rt, IF_ID_Rd;
output reg [5:0] Op_Code;
output reg [31:0] PC_Counter_Output;
output reg [15:0] Sign_Extend_Input;
output reg [4:0] IF_ID_RS_Hazard, IF_ID_RT_Hazard;
output reg [25:0] Jump_Offset;
input [31:0] Instruction;
input Enable, clk , Flush_Branch, Flush_Jump;
input [31:0] PC_Counter_Input;
always@(posedge clk)begin
    if(Flush_Branch == 1 | Flush_Jump == 1)
    begin
        Op_Code = 0;
        Read_Register_1 = 0;
        Read_Register_2 = 0;
        IF_ID_RS_Hazard = 0;
        IF_ID_RT_Hazard = 0;
        IF_ID_Rs = 0;
        IF_ID_Rt = 0;// two go into the ID_EX Pipeline module
        IF_ID_Rd = 0;
        Sign_Extend_Input = 0;
        PC_Counter_Output = 0;
        Jump_Offset= 0;
    end

    else if( Enable == 0)
    begin
        Op_Code = Op_Code;
        Read_Register_1 = Read_Register_1;
        Read_Register_2 = Read_Register_2;
        IF_ID_RS_Hazard = IF_ID_RS_Hazard;
        IF_ID_RT_Hazard = IF_ID_RT_Hazard;
        IF_ID_Rs = IF_ID_Rs;
        IF_ID_Rt =IF_ID_Rt;// two go into the ID_EX Pipeline module
        IF_ID_Rd = IF_ID_Rd;
        Sign_Extend_Input =Sign_Extend_Input;
        PC_Counter_Output = PC_Counter_Output;
        Jump_Offset=Jump_Offset;
    end
    else
    begin
        Op_Code = Instruction[31:26];
    end
end

```

```
Read_Register_1 = Instruction[25:21];
Read_Register_2 = Instruction[20:16];
IF_ID_RS_Hazard = Instruction[25:21];
IF_ID_RT_Hazard = Instruction[20:16];
IF_ID_Rs = Instruction[25:21];
IF_ID_Rt = Instruction[20:16]; // two go into the ID_EX Pipeline module
IF_ID_Rd = Instruction[15:11];
Sign_Extend_Input = Instruction[15:0];
PC_Counter_Output = PC_Counter_Input;
Jump_Offset = Instruction[25:0];
end
end
endmodule
```

Appendix M

```

module Instruction_Mem_Module(address_In, Instruction,clk);
input [31:0] address_In;
input clk;
output reg [31:0] Instruction;
reg[7:0] memfile[0:255];
initial begin

    {memfile[3 ],memfile[2 ],memfile[1 ],memfile[0 ]} = 32'hAC080000; // store word
    {memfile[7 ],memfile[6 ],memfile[5 ],memfile[4 ]} = 32'h00430824; //AND
    {memfile[3],memfile[2 ],memfile[1 ],memfile[0]} = 32'h00E80820;
    {memfile[7],memfile[6 ],memfile[5 ],memfile[4]} = 32'h80000003;
    {memfile[11],memfile[10 ],memfile[9 ],memfile[8]} = 32'h00430824;
    {memfile[15],memfile[14],memfile[13 ],memfile[12]} = 32'h00E80822;
    {memfile[19],memfile[18 ],memfile[17 ],memfile[16]} = 32'h00430824;

    {memfile[3],memfile[2 ],memfile[1 ],memfile[0]} = 32'h00E80822;
end
always@(posedge clk)begin
    Instruction = {memfile[address_In+3], memfile[address_In+2], memfile[address_In+1] ,
    memfile[address_In]};
end
endmodule

```

Appendix N

```

module Main_Control_Module(Jump_Signal, RegDst, Branch, MemRead, MemtoReg, ALUOp,
MemWrite, ALUSrc, RegWrite, Instruction_Op_Code);
output reg RegDst, Branch, MemRead, MemtoReg, MemWrite, ALUSrc, RegWrite, Jump_Signal;
output reg [1:0] ALUOp; // keep a 6 bit input for all registers
input [5:0] Instruction_Op_Code;
always@( Instruction_Op_Code)
begin
    if(Instruction_Op_Code == 0)
        begin
            RegDst = 1;
            Branch = 0;
            MemRead = 0;
            MemtoReg = 0;
            ALUOp = 2'b10;
            MemWrite = 0;
            ALUSrc = 0;
            RegWrite = 1;
            Jump_Signal=0;
        end

    else if( Instruction_Op_Code == 6'b10001)
        begin
            RegDst = 0;
            Branch = 0;
            MemRead = 1;
            MemtoReg = 1;
            ALUOp = 2'b00;
            MemWrite = 0;
            ALUSrc = 1;
            RegWrite = 1;
            Jump_Signal=0;
        end

    else if ( Instruction_Op_Code == 6'b101011)
        begin
            RegDst = 1'bx;
            Branch = 0;
            MemRead = 0;
            MemtoReg = 1'bx;
            ALUOp = 2'b00;
            MemWrite =1;
            ALUSrc = 1;
            RegWrite = 0;
            Jump_Signal=0;
        end
end

```

```

else if ( Instruction_Op_Code == 6'b000100)
    begin
        RegDst = 1'bx;
        Branch = 1;
        MemRead = 0;
        MemtoReg = 0;
        ALUOp = 2'b01; //from book page 579 Figure 4.18
        MemWrite = 0;
        ALUSrc = 0;
        RegWrite = 0;
        Jump_Signal=0;
    end
else if ( Instruction_Op_Code == 6'b00100)
    begin
        RegDst = 1'bx;
        Branch = 0;
        MemRead = 1'bx;
        MemtoReg = 0;
        ALUOp = 2'b00; //from book page 579 Figure 4.18, copied from lw and sw
since they are using add
        MemWrite = 0;
        ALUSrc = 1;
        RegWrite = 1;
        Jump_Signal=0;
    end
else if ( Instruction_Op_Code == 6'b000010)
    begin
        RegDst = 1'bx;
        Branch = 0;
        MemRead = 1'bx;
        MemtoReg = 0;
        ALUOp = 2'b00;
        MemWrite = 0;
        ALUSrc = 1;
        RegWrite = 1;
        Jump_Signal=1;
    end
end
end
endmodule

```


Appendix O

```

module MEM_WB_Pipeline_Module (
output reg [4:0] MEM_WB_Fowarding, MEM_WB_Rd_Register_Module,
output reg Regwrite_Output, MemtoReg_Output_Fowarding, MemtoReg_Output,
output reg [31:0] Data_Memory_Output_to_MUX,
output reg [31:0] ALU_Output_to_MUX,
input Regwrite_Input, MemtoReg_Input,
input [4:0] EX_MEM_RD,
input [31:0] Data_Memory_Output_IN,
input [31:0] ALU_Output_IN,
input clk,
);
always@(posedge clk)
begin
    Regwrite_Output = Regwrite_Input;
    MemtoReg_Output_Fowarding = MemtoReg_Input;
    MemtoReg_Output = MemtoReg_Input;
    MEM_WB_Fowarding = EX_MEM_RD;
    Data_Memory_Output_to_MUX = Data_Memory_Output_IN;
    ALU_Output_to_MUX = ALU_Output_IN;
    MEM_WB_Rd_Register_Module = EX_MEM_RD;
end
endmodule

```

Appendix P

```
module mux_1_module (out , a , b , c , control);
output reg [31:0] out;
input [31:0] a,b,c;
input [1:0] control;
always@(*)
begin
    if(control == 0)begin
        out = a;
    end
    else if (control == 2'b01)begin
        out = b;
    end
    else
        begin
            out = c;
        end
    end
end
Endmodule
```

Appendix Q

```
module Mux_2_to_1(out, a,b,control);
output reg [31:0]out;
input [31:0] a,b ;
input control;
always@(*)begin
if(control == 1)
begin
    out = b;
end
else
begin
out = a;
end
end
Endmodule
```

Appendix R

```
module Mux_2_to_1_5_bit(out , a , b , control);
output reg [4:0] out;
input [4:0] a, b;
input control;
always@(*)begin
    if(control == 1)
    begin
        out = b;
    end
    else
    begin
        out = a;
    end
end
end
endmodule
```

Appendix S

```

module Mux_Control_Module( ALU_Src_Out, ALUOP_Out, RegDst_Out, MemWrite_Out,
MemRead_Out, MemtoReg_Out, RegWrite_Out, ALUOP_In, RegDst_In, MemWrite_In,
MemRead_In, MemtoReg_In, RegWrite_In, Input_Hazard, ALU_Src_In);
output reg RegDst_Out, MemWrite_Out, MemRead_Out, MemtoReg_Out,
RegWrite_Out, ALU_Src_Out;
output reg [1:0] ALUOP_Out;
input RegDst_In, MemWrite_In, MemRead_In, MemtoReg_In, RegWrite_In, ALU_Src_In;
input [1:0] ALUOP_In;
input Input_Hazard;

```

```

always@(*)begin
    if(Input_Hazard == 0)
    begin
        RegDst_Out = 0;
        MemWrite_Out = 0;
        MemRead_Out = 0;
        MemtoReg_Out = 0;
        RegWrite_Out = 0;
        ALUOP_Out = 0;
        ALU_Src_Out = 0;
    end
    else
    begin
        RegDst_Out = RegDst_In;
        MemWrite_Out = MemWrite_In;
        MemRead_Out = MemRead_In;
        MemtoReg_Out = MemtoReg_In;
        RegWrite_Out = RegWrite_In;
        ALUOP_Out = ALUOP_In;
        ALU_Src_Out = ALU_Src_In;
    end
end
endmodule

```

Appendix T

```
module Mux_Last(out , a , b, control);
output reg [31:0] out;
input [31:0] a , b;
input control;
always@(*)
begin
    if(control == 1)
    begin
        out = a;
    end
    else
    begin
        out = b;
    end
end
Endmodule
```

Appendix U

```
module Program_Counter_Module(address_Out, enable, address_In,clk);
output reg [31:0] address_Out;
input [31:0] address_In;
input clk;
input enable;
initial
begin
address_Out = 0;
end
always@(posedge clk)
begin
    if(enable == 0)
    begin
        address_Out = 0;
    end

    else
    begin
        address_Out = address_In;
    end
end
end
endmodule
```

Appendix V

```

module Register_Module(read_data_1, read_data_2, read_reg_1, read_reg_2, write_reg, write_data,
regwrite, clk);
output reg [31:0] read_data_1, read_data_2;
input regwrite;
input [31:0] write_data;
input[4:0] read_reg_1, read_reg_2, write_reg;
input clk;
reg [31:0] regfile[0:31];
initial
begin
    regfile[32'd7] = 32'd2;
    regfile[32'd8] = 32'd2;
    regfile[32'd2] = 32'd2;
    regfile[32'd3] = 32'd3;
    regfile[32'd0] = 32'd0;
end
always@(negedge clk)begin
if (regwrite == 1)
    begin
        regfile[write_reg] = write_data;
    end
end

end
always@(read_reg_1, read_reg_2)
begin
    read_data_1 = regfile[read_reg_1];
    read_data_2 = regfile[read_reg_2];
end
end
Endmodule

```


Appendix W

```
module Shift_Left_2(in , out);  
output reg [31:0] out;  
input [31:0] in;  
always@(*)  
begin  
out = in << 2;  
end  
endmodule
```

Appendix X

```
module Sign_Extend_Module(Input_, Output_);  
output reg [31:0] Output_;  
input [15:0] Input_;  
always@(*)  
begin  
    Output_[31:16] = 0;  
    Output_[15:0] = Input_;  
end  
Endmodule
```

Appendix Y

```
module TB_File();  
reg clk;  
Top_Level_Module Top_Level(  
    .clk(clk));  
initial  
begin  
    clk = 0;  
end  
always  
#100 clk = ~clk;  
endmodule
```

Appendix Z

```

module Top_Level_Module( input clk);
    wire [31:0] Adder_Input;
    assign Adder_Input = 32'd4;
    wire [31:0] w1,w2,w7,w11,w12,w39,w40,w41,w44,w47,w46,w102,w105;
    wire [5:0] w3;
    wire w4,w16, w17,w18,w19,w20,w21,w22,w23,w24,w25,w45,w104;
    wire w48,w49,w99;
    wire [25:0] w100;
    wire [27:0] w101;
    wire [1:0] w26,w34;
    wire [4:0] w5,w6,w8,w9,w98;
    wire [15:0] w10;
    wire [4:0] w13,w14,w15,w37;
    wire w27,w28,w29,w30, w31,w32,w38,w36,w42;
    wire A1,A2,A3,A4,A5,A20;
    wire [1:0] A6,A13,A14;
    wire [4:0]A7,A8,A18,A19,A21;
    wire [3:0] A9;
    wire [31:0] A10,A12,A15,A16,A17;
    wire [31:0] A11;
    wire l0,l1,l2,l5,l6,l7,l8,l11,l16;
    wire [4:0] l9,l15;
    wire [31:0] l3,l4,l10,l12,l13,l14,l17;
    Program_Counter_Module Program_Counter_Module1 // done
    (.address_Out(w1),
    .enable(w38),
    .address_In(w105), // needs to come from the output of the MUX;
    .clk(clk));
    Mux_2_to_1 MUX_For_PC_2nd_to_Last( // leftmost mux
    .out(w39),
    .a(w12),
    .b(w40),
    .control(l16) // Control Input for PC counter input
    );
    Instruction_Mem_Module InstructionMem // done
    (.address_In(w1),
    .Instruction(w2), // output
    .clk(clk)
    );
    IF_ID_Pipeline_Module IF_ID_Pipeline // done
    (// need to add teh 26 bits for Jump
    .IF_ID_RS_Hazard(w5),
    .IF_ID_RT_Hazard(w6),
    .PC_Counter_Output(w7),
    .Op_Code(w3),

```

```

.Read_Register_1(w8),
.Read_Register_2(w9),
.IF_ID_Rs(w13),
.IF_ID_Rt(w14),
.IF_ID_Rd(w15),
.Sign_Extend_Input(w10),
.Enable(w4),
.Instruction(w2),
.clk(clk),
.Flush_Branch(l16),
.Flush_Jump(w104),
.Jump_Offset(w100),
.PC_Counter_Input(w12) // 32 bit adder
);
Shift_Left_Input_26 Shift_Left_Jump_26(
.out(w101) ,
.in(w100));//
Concatenation_28_32 Concatenation_26_32_Jump(
.out(w102),
.a(w101) ,
.b(w7)// b should be w7);
Mux_Last MUX_For_PC_Last(
.out(w105) ,
.a(w102) ,
.b(w39),
.control(w104)
);

Sign_Extend_Module Sign_Extend (
    .Input_(w10),
    .Output_(w11) );

Shift_Left_2 Shift_Left_
(.in(w11),
.out(w41));

Adder_32_bit Adder_32_bit1
(.out(w40),
.a(w7),
.b(w41));
Adder_32_bit Adder_Before_IF_ID
(.out(w12),
.a(w1),
.b(Adder_Input));

Main_Control_Module Main_ControlM1
(
    . Instruction_Op_Code(w3),

```

```

        . RegDst(w17),
        . Branch(w18),
        . MemRead(w19),
        . MemtoReg(w20),
        . MemWrite(w21),
        . RegWrite(w23),
        . ALUOp(w26),
        . ALUSrc(w45),
        . Jump_Signal(w104)
    );

```

```

Mux_Control_Module Mux_Control_Module1(
    .ALUOP_Out(w34),
    .RegDst_Out(w32),
    .MemWrite_Out(w31),
    .MemRead_Out(w30),
    .MemtoReg_Out(w28),
    .RegWrite_Out(w27),
    .ALU_Src_Out(w48),
    .ALUOP_In(w26),
    .RegDst_In(w17),
    .MemWrite_In(w21),
    .MemRead_In(w19),
    .MemtoReg_In(w20),
    .RegWrite_In(w23),
    .ALU_Src_In(w45),
    .Input_Hazard(w16)
);

```

```

ID_EX_Pipeline_Module ID_EX_Module1 (
    . Regwrite_Input(w27),
    . MemtoReg_Input(w28),
    . MemRead_Input(w30),
    . MemWrite_Input(w31),
    . RegDst_Input(w32),
    . ALUOp_Input(w34),
    . Sign_Extend_Input (w11) ,
    . IF_ID_Rs (w13),
    . IF_ID_Rt (w14),
    . IF_ID_Rd (w15),
    . Read_Data_1_Input (w46),
    .Read_Data_2_Input (w47),
    .clk(clk),
    . ALU_Src_In(w48),
    .Regwrite_Output (A1),
    . MemtoReg_Output (A2),
    . MemRead_Output (A4),

```

```

    . MemWrite_Output (A5),
    . RegDst_Output(A20),
    . ALUOp_Output(A6),
    . Sign_Extend_Output(A11),
    . ID_EX_Rs_Fowarding (A7),
    . ID_EX_Rt_Fowarding (A8),
    . ID_EX_Rt_MUX(A18),
    . ID_EX_Rd_MUX(A19),
    . Read_Data_1_Output(A12),
    . Read_Data_2_Output(A17),
    . ALU_Src_Out(w49) );

```

```

Register_Module Register1 (
    . read_reg_1 (w8) ,
    .read_reg_2 (w9) ,
    .write_reg (w37),
    .write_data (l12),
    .regwrite(w36),
    .clk(clk),
    .read_data_1 (w46),
    .read_data_2 (w47));

```

```

Comparator Comparator_for_register_Module(
    .out (w99),
    . a(w46) ,
    .b(w47));

```

```

AND_Gate And_Gate_Branch(
    .out(l16) ,
    .a(w18) ,
    .b(w99)
);

```

```

Hazard_Unit_Module Hazard_module1 (
    . IF_ID_RS(w5),
    . IF_ID_RT(w6),
    . ID_EX_RT(A8),
    . ID_EX_Mem_Read(A4),
    . IF_ID_Enable(w4),
    . PC_Write_Enable(w38),
    . Mux_Output(w16));

```

```

mux_1_module Forward_A_Mux (
    .a(A12),
    . b(l12),
    .c(l3),
    . control(A13),
    .out(A15));

```

```

mux_1_module Forward_B_Mux (
    .a(A17),
    .b(l12),
    .c(l3),
    .control(A14),
    .out(A16));

Mux_2_to_1 MUX_ALU_Src(
    .out(w44), // goes out to ALU
    .a(A16), // forwarding unit B
    .b(A11), // sign extend input
    .control(w49) // ALU Src Signal);

mux_3_module Bottom_Mux_After_ID_EX (
    .ID_EX_RT(A18),
    .ID_EX_RD(A19),
    .RegDst_Output(A20),
    .Mux3_output(A21));

Mux_2_to_1_5_bit Bottom_Mux_After_ID_EX(
    .out(A21),
    .a (A18),
    .b (A19),
    .control(A20));

Forward_Unit_Module Forward_Module1 (
    .ID_EX_RS (A7),
    .ID_EX_RT (A8),
    .EX_MEM_RD (l9), // Outputs from Luigi
    .MEM_WB_RD (l15),
    .EX_MEM_Reg_Write(l5),
    .MEM_WB_Reg_Write(w36),
    .forward_A(A13),
    .forward_B(A14) );

ALU_Module ALU1 (
    .input_1(A15),
    .input_2(w44),
    .control_input(A9),
    .output_ (A10) );

ALU_Control_Module ALU_ControlM1 (
    .Function_Code(A11),
    .ALU_Op_Input(A6),
    .ALU_Op_Output(A9) );

```



```

EX_MEM_Pipeline_Module EX_MEM_Module1 (
    . RegWrite_Input (A1),
    . MemtoReg_Input (A2),
    . MemRead_Input (A4),
    . MemWrite_Input (A5),
    . ID_EX_MUX(A21),
    . ALU_Result_Input (A10),
    .RT_32_Bit_Input(A17),
    .clk(clk),
    .RT_32_Bit_Output(117),
    . RegWrite_Output (15),
    . MemtoReg_Output (16),
    . MemRead_Output(11),
    . MemWrite_Output(12),
    . EX_MEM_RD_Fowarding (19),
    . EX_MEM_RD_Next_Pipeline(w98),
    . ALU_Result_Output(13) );

```

```

Mux_Last Mux_Last1(
    .out(112),
    .a(113),
    .b(114),
    .control(111));

```

```

Data_Memory_Module Data1(
    .data_output(110),
    .address_input(13),
    .write_data(117),
    .memWrite(12),
    .memRead(11),
    .clk(clk));

```

```

MEM_WB_Pipeline_Module MEM_WB_Module1 (
    .Regwrite_Input(15),
    .MemtoReg_Input(16),
    .EX_MEM_RD(w98),
    .Data_Memory_Output_IN(110),
    .ALU_Output_IN(13),
    .clk(clk),
    .MEM_WB_Fowarding(115),
    .MEM_WB_Rd_Register_Module(w37),
    .Regwrite_Output(w36),
    .MemtoReg_Output(111),
    .Data_Memory_Output_to_MUX(113),
    .ALU_Output_to_MUX(114));
endmodule

```